

S.No. : 7

BEC 3201

No. of Printed Pages : 05

Following Paper ID and Roll No. to be filled in your Answer Book.

PAPER ID : 33402

Roll
No.

--	--	--	--	--	--	--	--	--	--

B. Tech. Examination 2021-22

(Even Semester)

BASIC ELECTRONICS ENGINEERING

Time : Three Hours]

[Maximum Marks : 60

Note :- Attempt all questions.

SECTION – A

1. Attempt all parts of the following : $8 \times 1 = 8$
 - (a) Distinguish between Avalanche and Zener breakdown mechanisms.
 - (b) What do you mean by Doping? Describe its need.
 - (c) Define threshold voltage for an E-MOSFET. Also define I_{DSS} for an JFET.
 - (d) Explain FET as voltage variable resistor.

[P. T. O.]

- (e) Convert $(6089.25)_{10} \rightarrow (?)_8$.
- (f) Explain need for modulation.
- (g) Enlist the characteristics of an ideal op-amp.
- (h) Explain Barkhausen criterion for oscillation.

SECTION – B

2. Attempt any two parts of the following : $2 \times 6 = 12$


- (a) What do you mean by rectification? With help of neat circuit diagrams, explain working of a full wave bridge rectifier and calculate ripple factor.
- (b) Give a sketch of the basic structure of n-channel enhancement type MOSFET. Explain its operation and characteristics. Discuss pinch off voltage.
- (c) What are the basic elements of communication system? Explain communication system with the help of block-diagram.
- (d) Define CMRR and slew rate. Draw the circuit diagram of differentiator using op-amp and derive the expression for voltage gain.

SECTION - C

Note :- Attempt all questions from this section. 10×4

3. Attempt any two parts of the following :


- (a) Explain VI characteristics of a P-N junction diode under forward and reverse bias conditions.
- (b) Give a short note on any **two** of the following :
 - (i) LED
 - (ii) LCD
 - (iii) Solar Cell
- (c) Determine V_L , V_R , I_Z and I_R for given network :

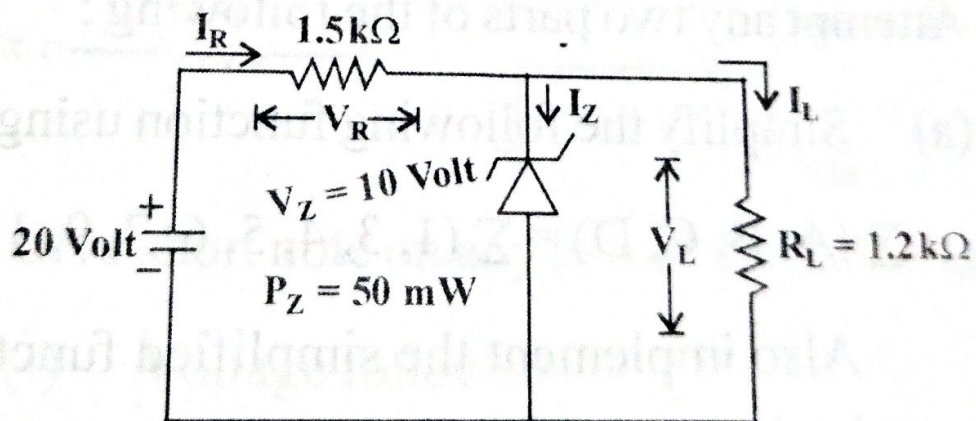

4. Attempt any two parts of the following :

- (a) Explain voltage divider bias configuration for BJT. Find I_C and V_{CE} for given circuit if $\beta = 100$:

[P. T. O.]

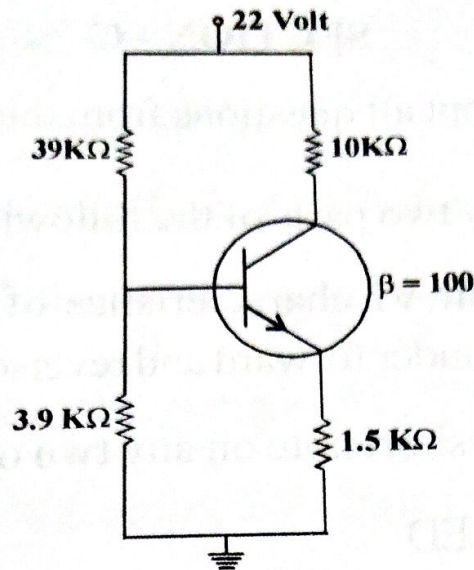

(b) Draw and explain input and output characteristics of a BJT in CE configuration.

(c) Explain working principle of NPN bipolar junction transistor.

5. Attempt any two parts of the following :

(a) Simplify the following function using K map :

$$\Sigma (A, B, C, D) = \Sigma (1, 3, 4, 5, 6, 7, 9, 11, 13, 15)$$

Also implement the simplified function using basic gates only.

(b) By showing all the calculations, do as directed :


(i) $(110110.011)_2 = (?)_{16}$

(ii) $(231.36)_{10} = (?)_2$

- (c) What do you mean by amplitude modulation? Explain with help of proper wave forms.

6. Attempt any two parts of the following :

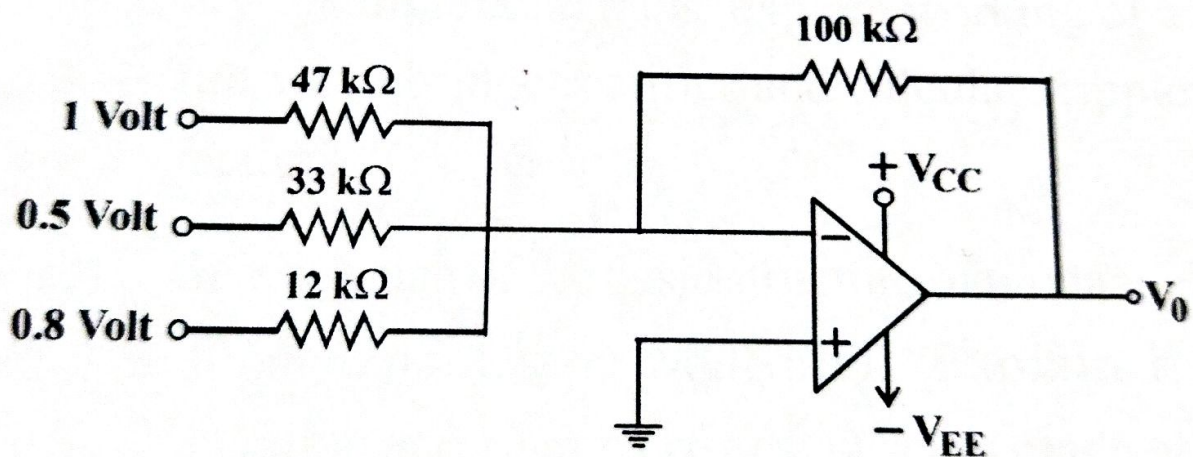- (a) Explain op-amp as a summer with necessary calculations and diagram. Why open loop op-amp configuration are not used in linear applications.
- (b) Find output voltage of the following op-amp circuit :



- (c) Give short note on any two of the following :
- (i) Voltage follower
 - (ii) Inverting amplifier
 - (iii) Op-amp as an integrator